

Figure: Inputted Sine Wave

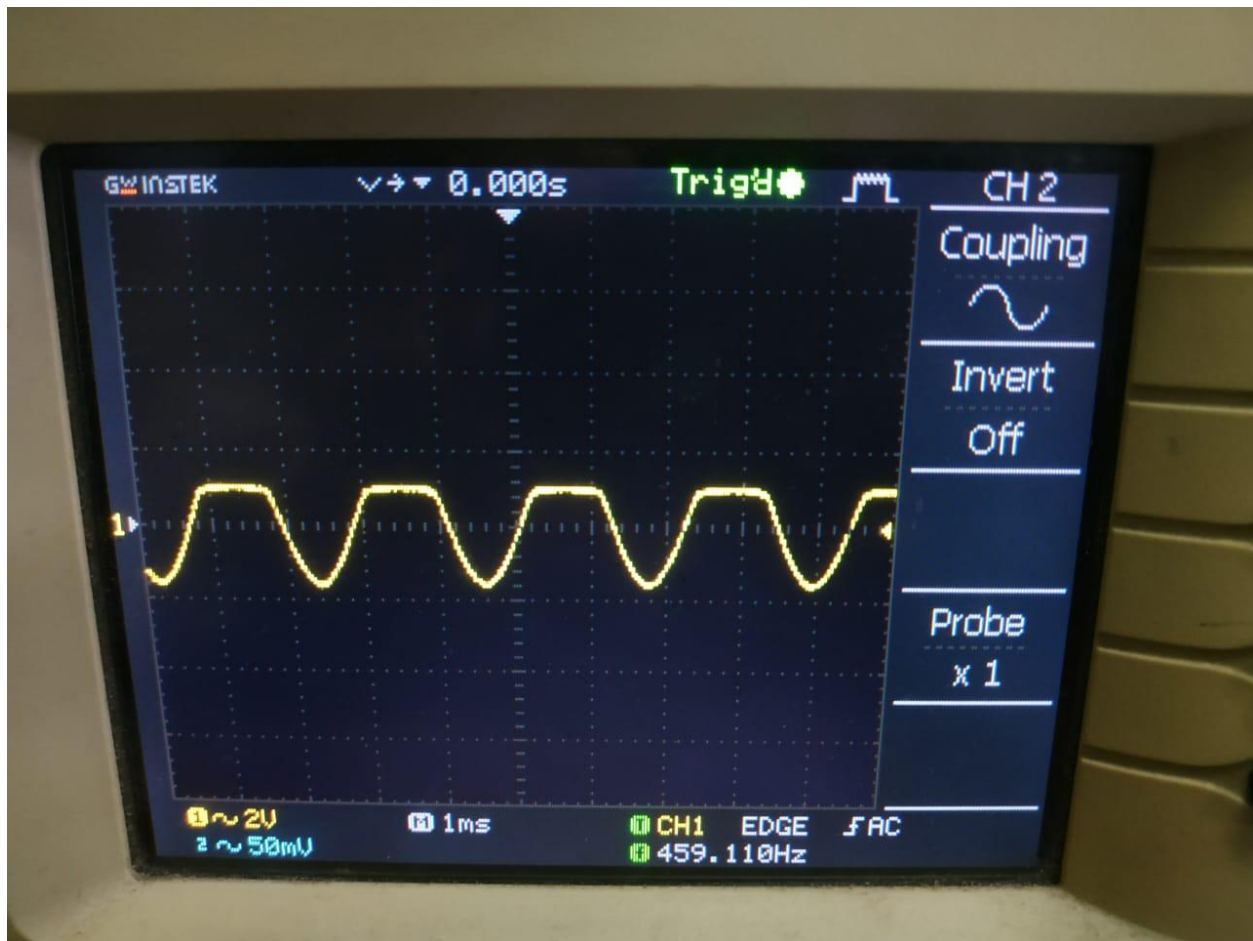


Figure: Output Waveform of Shunt Positive Clipper Circuit

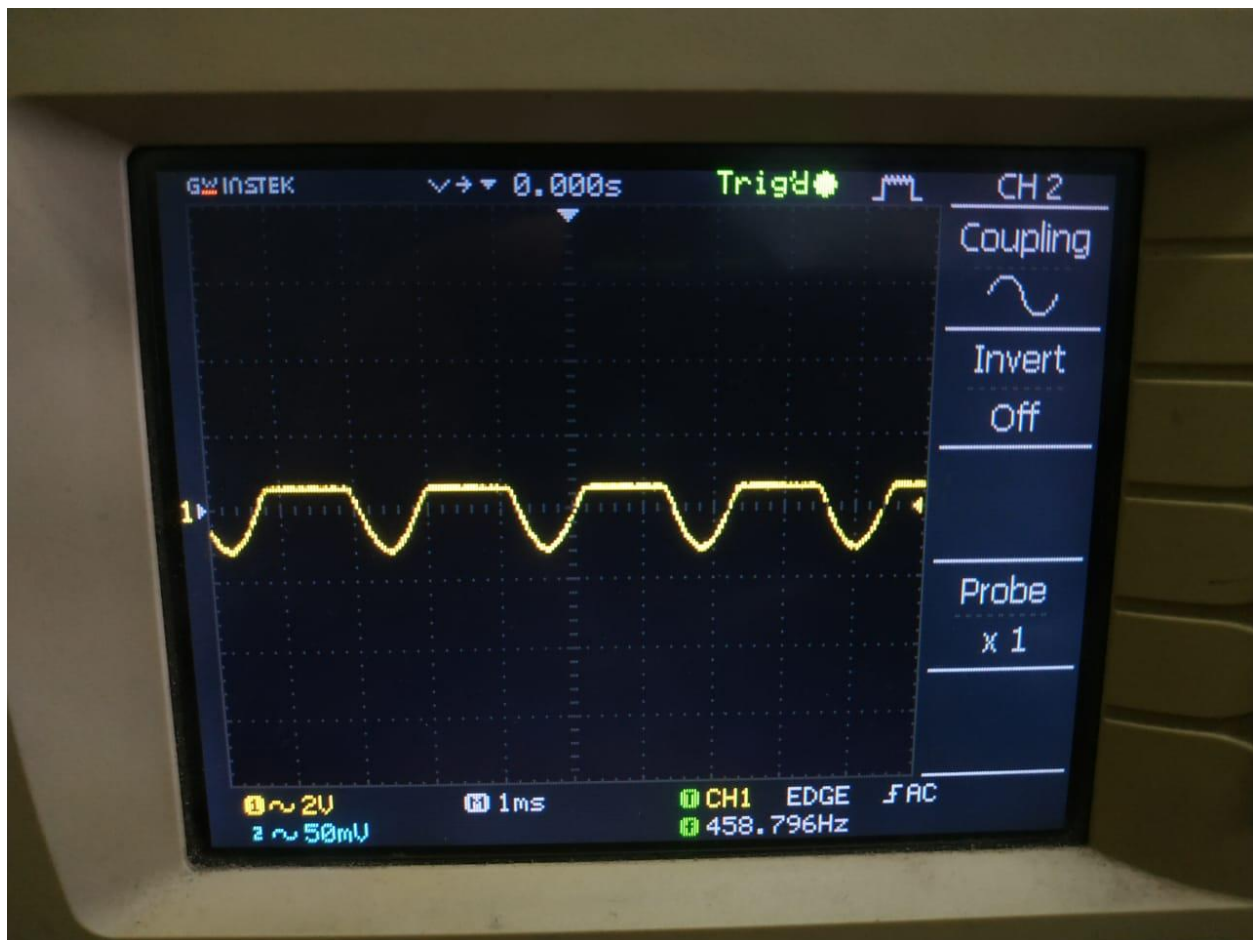


Figure: Output Waveform of Series Positive Clipper Circuit